

# Sub-Group: A-7

## Experiment 5: Study of 555 Timer IC

Sayan Karmakar  
22MS163

### 1 Aim:

Study of 555 Timer IC as Astable multivibrator with different frequency.

### 2 Theory:

#### Pin Functions:

1. **Trigger Input:** When it is less than  $V_S/3$  it makes the output high  $V_S$ . It monitors the discharging of timing capacitor in astable circuit.
2. **Threshold Input:** When it is greater than  $2V_S/3$ , it makes the output low (0 V). But this only happens if the trigger input is more than  $V_S/3$ . If the trigger input is low then it forces the output to be high. This input monitors the charging of time capacitor in astable and monostable circuit.
3. **Reset Input:** When it is less than 0.7 V, it makes the output low(0 V), overriding other inputs. When it is unnecessary it should be connected to the source voltage.
4. **Control Input:** If there is a need to change the threshold voltage which is normally set to  $2V_S/3$ , usually this is connected to 0 V with a very low capacitor of  $0.01 \mu\text{F}$  to avoid electrical noise.
5. **Discharge Pin:**

#### 2.1 555/ 556 Astable Circuit:

Time period ( $T$ ) of the square wave is the time for one complete cycle. And frequency ( $f$ ) of the wave is no. of complete cycles per second.

$$T = 0.7(R_1 + 2R_2)C_1$$
$$f = \frac{1.4}{(R_1 + 2R_2)C_1}$$

Time period can be split into two part, when the output is high, **mark time** ( $T_m$ ) and when the output is low, **space time** ( $T_s$ ).

$$\begin{aligned} T_m &= 0.7(R_1 + R_2)C_1 \\ T_s &= 0.7R_2C_1 \end{aligned}.$$

### 3 Data and Analysis