

# Sub-Group: A-7

## Experiment 5: Study of 555 Timer IC

Sayan Karmakar  
22MS163

### 1 Aim:

Study of 555 Timer IC as Astable multivibrator with different frequency.

### 2 Theory:

#### Pin Functions:

1. **Trigger Input:** When it is less than  $V_S/3$  it makes the output high  $V_S$ . It monitors the discharging of timing capacitor in astable circuit.
2. **Threshold Input:** When it is greater than  $2V_S/3$ , it makes the output low (0 V). But this only happens if the trigger input is more than  $V_S/3$ . If the trigger input is low then it forces the output to be high. This input monitors the charging of time capacitor in astable and monostable circuit.
3. **Reset Input:** When it is less than 0.7 V, it makes the output low(0 V), overriding other inputs. When it is unnecessary it should be connected to the source voltage.
4. **Control Input:** If there is a need to change the threshold voltage which is normally set to  $2V_S/3$ , usually this is connected to 0 V with a very low capacitor of  $0.01 \mu\text{F}$  to avoid electrical noise.
5. **Discharge Pin:**

#### 2.1 555/ 556 Astable Circuit:

Time period ( $T$ ) of the square wave is the time for one complete cycle. And frequency ( $f$ ) of the wave is no. of complete cycles per second.

$$T = 0.7(R_1 + 2R_2)C_1$$
$$f = \frac{1.4}{(R_1 + 2R_2)C_1}$$

Time period can be split into two part, when the output is high, **mark time** ( $T_m$ ) and when the output is low, **space time** ( $T_s$ ).

$$\begin{aligned} T_m &= 0.7(R_1 + R_2)C_1 \\ T_s &= 0.7R_2C_1 \end{aligned}.$$

### 3 Data and Analysis

Table 1: Experimental and Theoretical Time Constants

$C_1(\mu\text{F})$	$R_1$	$R_2$	$f_{\text{theo}}(\text{kHz})$	$T_m(\mu\text{s})$	$T_s(\text{ps})$	$T(\text{ps})$	$f_{\text{expt}}(\text{kHz})$	Error(%)
0.001	1	10	$6.667 \times 10^1$	9.5	8.5	$1.8 \times 10^1$	$5.556 \times 10^1$	16.67
0.001	10	100	6.667	$8.4 \times 10^1$	$7.4 \times 10^1$	$1.58 \times 10^2$	6.329	5.06
0.001	100	1000	$6.667 \times 10^{-1}$	$7.8 \times 10^2$	$7.0 \times 10^2$	$1.480 \times 10^3$	$6.757 \times 10^{-1}$	1.35
0.01	1	10	6.667	$7.6 \times 10^1$	$7.0 \times 10^1$	$1.46 \times 10^2$	6.849	2.74
0.01	10	100	$6.667 \times 10^{-1}$	$8.2 \times 10^2$	$7.8 \times 10^2$	$1.600 \times 10^3$	$6.250 \times 10^{-1}$	6.25
0.01	100	1000	$6.667 \times 10^{-2}$	$8.4 \times 10^3$	$7.6 \times 10^3$	$1.600 \times 10^4$	$6.250 \times 10^{-2}$	6.25
0.1	1	10	$6.667 \times 10^{-1}$	$6.4 \times 10^2$	$6.0 \times 10^2$	$1.280 \times 10^3$	$7.813 \times 10^{-1}$	17.19
0.1	10	100	$6.667 \times 10^{-2}$	$7.2 \times 10^3$	$6.8 \times 10^3$	$1.400 \times 10^4$	$7.143 \times 10^{-2}$	7.14
0.1	100	1000	$6.667 \times 10^{-3}$	$7.4 \times 10^4$	$7.0 \times 10^4$	$1.440 \times 10^5$	$6.944 \times 10^{-3}$	4.16
1	1	10	$6.667 \times 10^{-2}$	$7.0 \times 10^3$	$6.4 \times 10^3$	$1.340 \times 10^4$	$7.463 \times 10^{-2}$	11.94
1	10	100	$6.667 \times 10^{-3}$	$7.2 \times 10^4$	$6.6 \times 10^4$	$1.380 \times 10^5$	$7.246 \times 10^{-3}$	8.69
1	100	1000	$6.667 \times 10^{-4}$	$7.0 \times 10^5$	$6.4 \times 10^5$	$1.340 \times 10^6$	$7.463 \times 10^{-4}$	11.90
10	1	10	$6.667 \times 10^{-3}$	$7.4 \times 10^4$	$6.8 \times 10^4$	$1.420 \times 10^5$	$7.042 \times 10^{-3}$	5.63
10	10	100	$6.667 \times 10^{-4}$	$8.0 \times 10^5$	$7.2 \times 10^5$	$1.520 \times 10^5$	$6.579 \times 10^{-4}$	1.30
10	100	1000	$6.667 \times 10^{-5}$	$7.5 \times 10^6$	$6.0 \times 10^6$	$1.350 \times 10^7$	$7.407 \times 10^{-5}$	11.00