

Experiment 01: Study of Zener Diode and IC 7805

Sagnik Seth
22MS026

Sayan Karmakar
22MS163

1 Aim

- To study Zener diode as a voltage regulator.
- To study IC 7805 as a voltage stabiliser.

2 Theory

3 Data and Calculation

4 Conclusion