

Sub-Group: A-7

Experiment 1: Study of Zener Diode and IC7805

Sayan Karmakar
22MS163

1 Aim

Aim of this experiment is to

- Study voltage regulation of Zener diode.
- Study voltage regulation of IC7805.

2 Theory

2.1 Zener Diode:


Zener diode is a general purpose diode that acts as a normal diode when connected to the circuit in forward bias but when it is connected in reverse bias it acts as a voltage regulator for a wide range of currents.

In forward bias a Zener diode has the same I-V characteristics as a regular diode i.e. there is a knee voltage after which current starts increasing exponentially with voltage. In reverse bias initially for any voltage the current remains constant. This is called saturation current. But increasing the voltage further causes it to reach the reverse bias breakdown region. When breakdown voltage is reached, even a slight change in voltage can cause a very large increase in current through the Zener diode. This change in saturation current to breakdown is smooth but after this the current increases rapidly. Because of this, voltage remains almost constant throughout this increase in current. This is the reason, Zener diode is used as a voltage regulator. As the current increases, the power dissipation in the Zener diode also increases. So for very current, due to excessive heat the Zener diode can be damaged. So they have a maximum current rating. And it should be used below that current level.

Purpose of a voltage regulator is to supply constant voltage to any load present in the circuit in spite of fluctuations in the supply voltage or load current. To do this, the Zener diode is used in parallel to the load. So if the Zener diode reaches breakdown region and the current through the Zener diode is less than maximum current then

voltage across the diode will remain almost constant and the same thing will happen to the load.

Figure 1: Circuit Diagram for Zener Diode

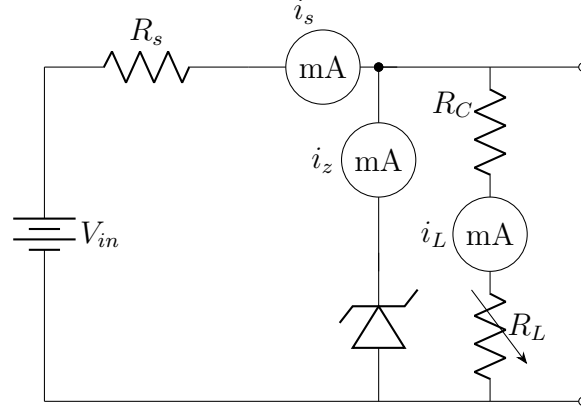


2.2 IC:

Using a Zener diode as a voltage regulator has a major drawback. Regulation is not perfect as the voltage is not really constant, it changes very slowly with the current. Also the maximum current that can flow through the diode without damaging it is quite low. So, tackle this, IC based voltage regulators are used.

In this experiment, IC7805 is used. This has three pins. These pins are input, output, and ground. The last two digits of the number represent the voltage it regulates. While maximum current in Zener diode is in the milliampere range, for IC7805 it is 1 ampere. It also has thermal overload protection and short circuit protection. The circuit diagram is shown below.

Figure 2: Circuit Diagram for IC7805

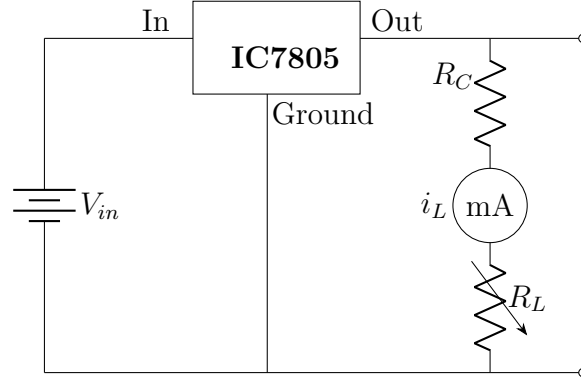

3 Data and Calculation

For both Zener diode and IC7805 there are two types of regulation - line regulation and load regulation. In line regulation the load resistance R_L and series resistance R_s is kept fixed and the input voltage is varied. And in load regulation, input voltage V_m remains constant but the load resistance R_L is varied. In this experiment data collection has been done for both the regulations in case of Zener diode and IC7805.

3.1 Zener Diode:


3.1.1 Line Regulation

In case of line regulation for Zener diode, load resistance was kept at $R_L = 1.1 \text{ k}\Omega$. Variation of output voltage V_o , current across Zener I_z and current in the circuit I_s with respect to the change in input voltage is shown in the following table:

V_i (V)	I_s (mA)	I_z (mA)	V_o (V)
0	0	0.00000	0.01
0.6	0	0.00000	0.4
1	0.12	0.00000	0.69
1.6	0.23	0.00000	1.02
2.1	0.35	0.00000	1.31
2.4	0.46	0.00000	1.52
3	0.12	0.00000	1.85
3.5	0.23	0.00000	2.16
3.9	0.58	0.00000	2.43
4.5	0.69	0.00000	2.77
5	0.81	0.00002	3.09
5.4	0.93	0.00008	3.31
6	1.05	0.00023	3.68
6.5	1.18	0.00040	3.92
7	1.27	0.00083	4.23
7.5	1.39	0.00161	4.57
8	1.51	0.00337	4.87
8.5	1.63	0.00637	5.16
8.9	1.74	0.01132	5.40
9.5	1.86	0.01666	5.71
10	1.98	0.03700	6.05
10.5	1.58	0.04000	6.35
11	2.11	0.10000	6.50
11.5	2.30	0.30000	6.53
11.9	2.50	0.50000	6.57


V_i (V)	I_s (mA)	I_z (mA)	V_o (V)
12.5	2.74	0.70000	6.55
13	3.01	1.00000	6.56
13.6	3.24	1.30000	6.57
13.9	3.41	1.40000	6.57
14.5	3.67	1.70000	6.57
15	3.89	1.90000	6.58

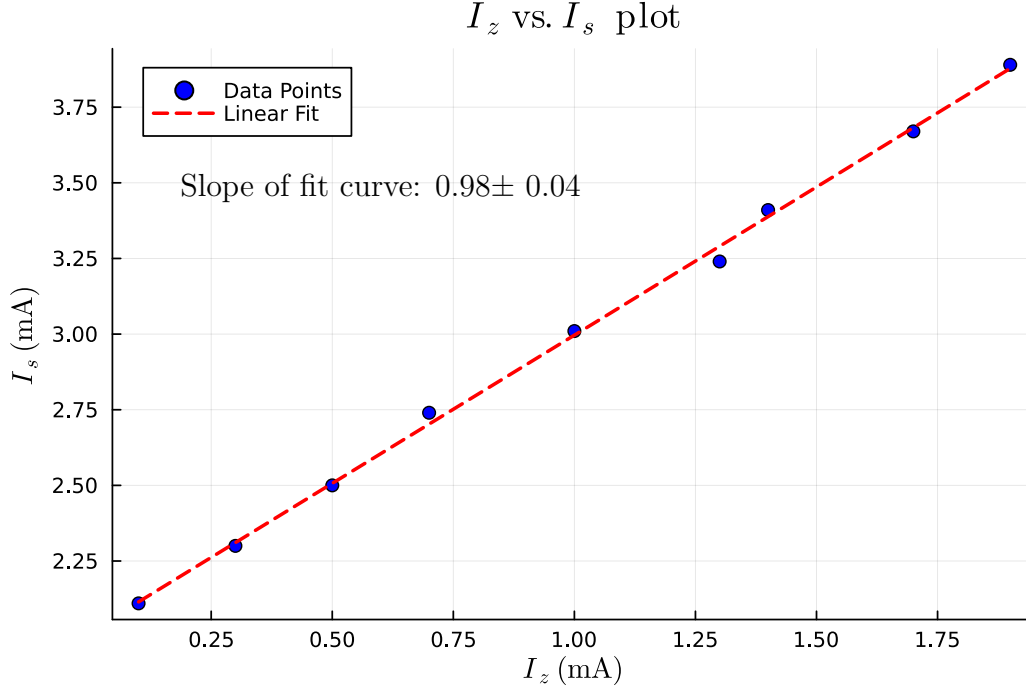We plotted I_s and I_z from this table. From this graph we see that I_s and I_z are proportional to each other. Here the graph was plotted for V_i more than 10.5 V. Before this the current is very small and zero. Around 10.5 V the current increases rapidly. We fitted this data with linear fit. Slope of this curve is 0.98 ± 0.04 . From this we can say that $\delta I_z = \delta I_s$.



In the following graph, we plotted V_{out} and V_{in} . From this plot, we can see that before V_{in} reaches 10.5 V, the graph is increasing. But after that the graph becomes constant. This means the corresponding V_{out} is the breakdown voltage. So, the breakdown voltage is

$$V_b = 6.55 \text{ V.}$$

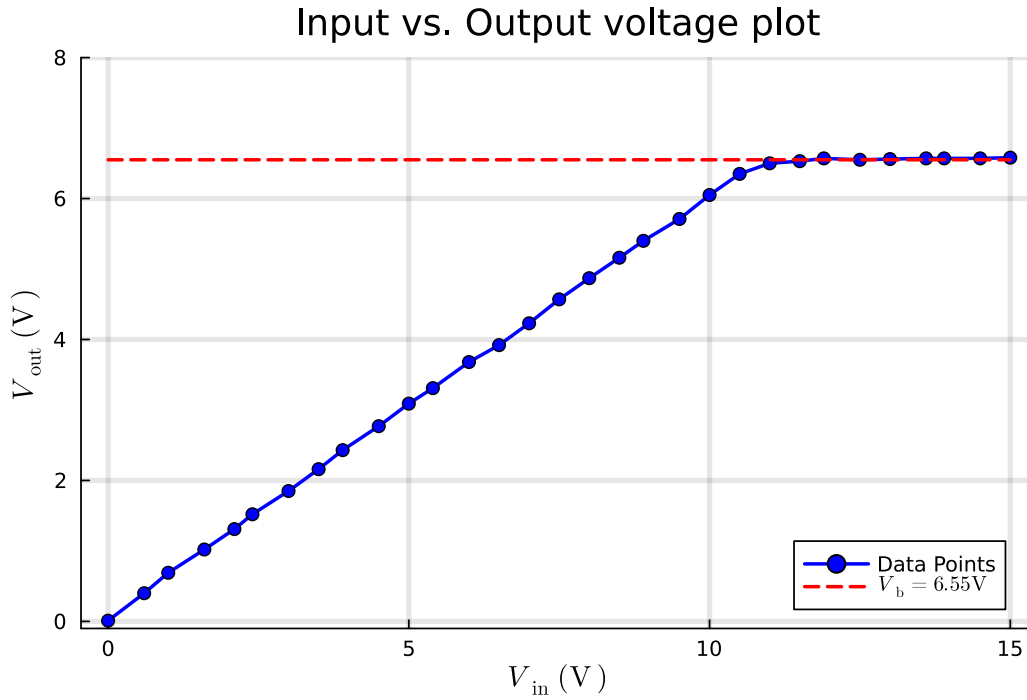

3.1.2 Load Regulation

The load regulation of Zener diode was studied in two cases. In the first case it was without R_c and in the second case with R_c set to $2.2\text{ k}\Omega$.

Without R_c :

In this case, the input voltage was fixed at $V_i = 15\text{V}$. The load resistance was changed using a potentiometer. The following table contains output voltage, current through Zener diode and the load current corresponding to each load resistance.

R_L (k Ω)	I_L (mA)	I_z (mA)	V_o (V)
0.007	6.92	0	0.2
0.057	6.76	0	0.5
0.106	6.61	0	0.9
0.153	6.5	0	1.2
0.203	6.36	0	1.4
0.249	6.25	0	1.7
0.304	6.11	0	2.1
0.354	6.02	0	2.3
0.396	5.92	0	2.6
0.452	5.78	0	2.8
0.513	5.64	0	3.1
0.551	5.53	0	3.3

R_L (k Ω)	I_L (mA)	I_z (mA)	V_o (V)
0.609	5.44	0	3.5
0.655	5.34	0	3.7
0.713	5.24	0	3.9
0.751	5.16	0	4.1
0.802	5.06	0	4.3
0.856	5	0	4.5
0.906	4.92	0	4.7
0.955	4.84	0	4.9
1.017	4.73	0	5


Breakdown voltage calculated in the first part was found to 6.55 V. Here we see that maximum output voltage reached without using R_c is 5 V. This is less than the breakdown voltage, so we are getting zero current.

With R_c : 2.2 k Ω


The following table is with $R_c = 2.2$ k Ω . We tabulated the same data as in last table.

R_L (k Ω)	I_L (mA)	I_A (mA)	V_o (V)
0.065	2.83	1.22	6.4
0.107	2.78	1.33	6.4
0.154	2.72	1.41	6.4
0.177	2.68	1.46	6.4
0.242	2.63	1.41	6.6
0.312	2.55	1.45	6.52
0.317	2.49	1.55	6.6
0.406	2.46	1.67	6.6
0.467	2.4	1.64	6.6
0.532	2.35	1.71	6.7
0.61	2.28	1.76	6.6
0.672	2.23	1.81	6.4
0.713	2.2	1.9	6.6
0.752	2.17	1.94	6.6
0.815	2.13	1.98	6.6
0.902	2.07	2	6.6
0.951	2.04	1.94	6.6
1.033	1.98	2.14	6.6

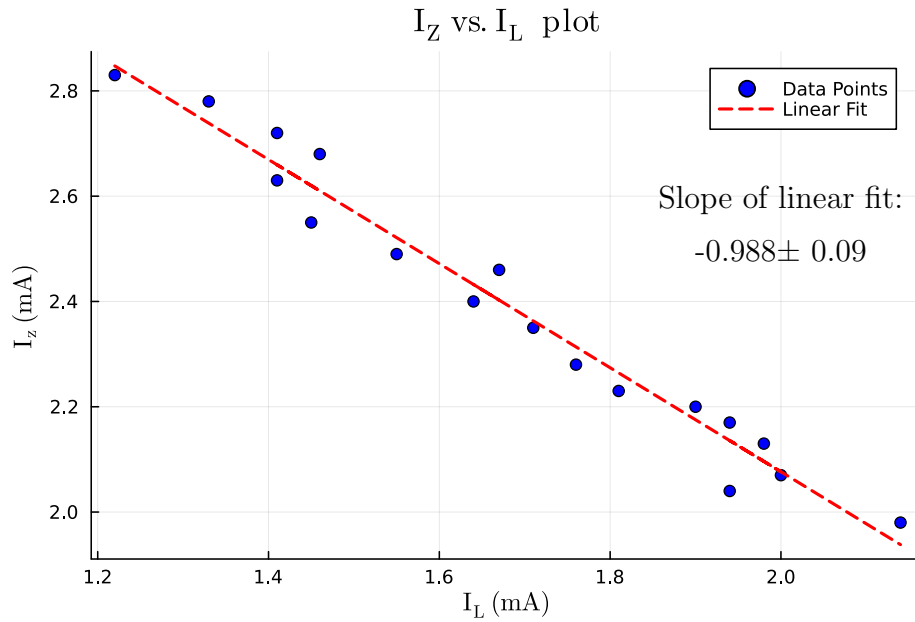In the following plot, we plotted V_o and R_L . Here we see that the diode has already reached breakdown region. So V_o is constant and remains about 6.6 V.



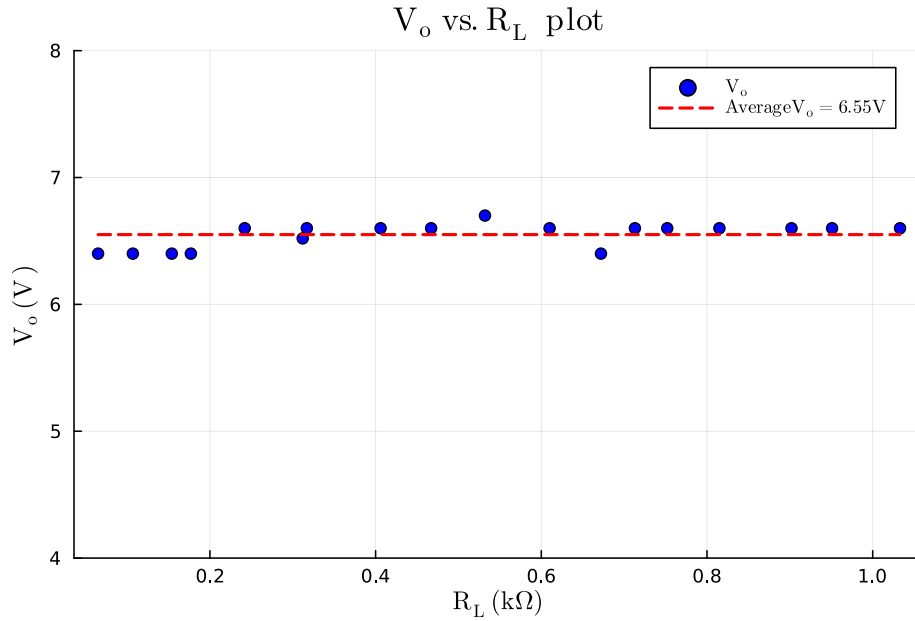In the following plot, we plotted I_Z and I_L . The fitting line for this graph has slope -0.98 ± 0.09 . This satisfies $\delta I_Z = -\delta I_L$.



3.2 IC7805


3.2.1 Line Regulation

For line regulation in IC7805, resistance $R_L + R_C$ was kept at $2.2 \text{ k}\Omega$. The following table has value of current through the load and output voltage corresponding to different

value of input voltage V_{in} .

$V_{in}(V)$	$I_L(mA)$	$V_o(V)$
0	0	0
0.12	0	0
0.13	0	0
0.14	0.01	0.01
0.15	0.76	0.18
1.6	0.85	0.38
1.7	1.04	0.46
1.8	1.17	0.51
2.5	1.76	0.77
3	1.02	2.23
3.4	1.22	2.66
4	1.47	3.2
4.5	1.67	3.62
5.1	1.92	4.17
5.4	2.03	4.41
5.5	2.12	4.6
5.8	2.21	4.79
5.9	2.25	4.89
6	2.3	4.99
6.5	2.31	5.0
7.1	2.3	5.0
7.5	2.3	5.0
8	2.3	5.0
9	2.3	5.0
10	2.3	5.0
11	2.3	5.0
12	2.3	5.0

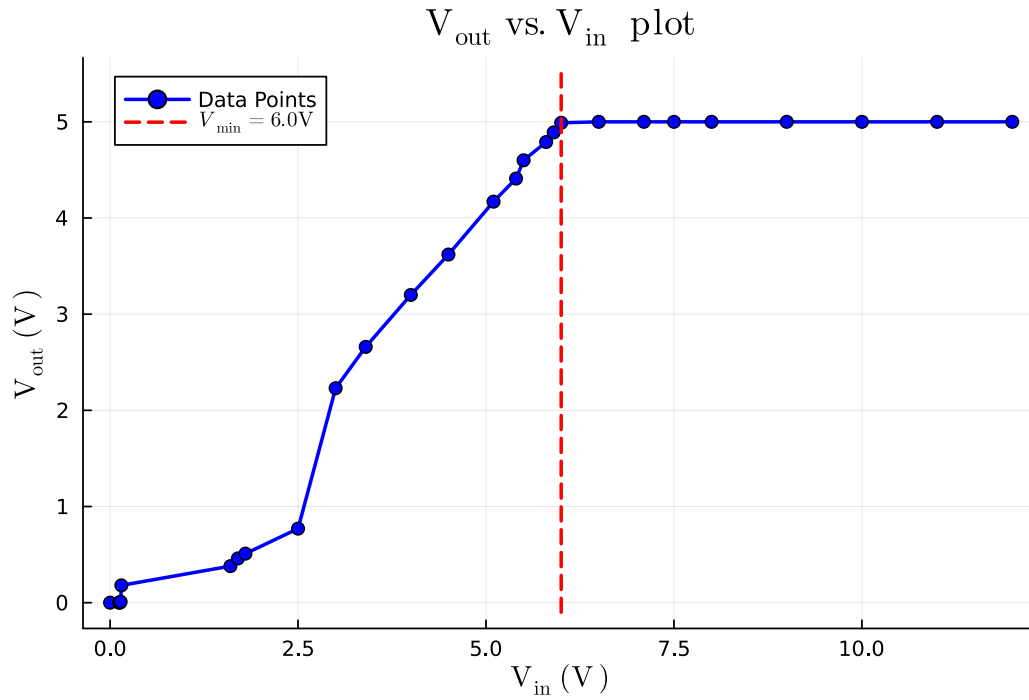The following plot contains graph of V_{in} vs V_{out} . We can see that after input voltage reaches 6 V, output voltage becomes 5 V. So, IC works as voltage regulator when the input voltage reaches 6 V. As the last two digits of the IC7805 is 05 the output voltage should be 5 V. From the table we can see that the output voltage is 5 V.




3.2.2 Load Regulation

While checking load regulation, we fixed input voltage as 15 V. The load resistance was varied using potentiometer. The following table contains i_L and V_o corresponding to different values of resistance R_L .

R_L (k Ω)	i_L (A)	V_o (V)
0.001	2.35	5.09
0.025	2.29	5.03
0.033	2.27	4.98
0.082	2.23	5.02
0.143	2.16	5.00
0.196	2.12	5.00
0.28	2.07	5.06
0.342	2.00	5.03
0.403	2.08	5.42
0.492	1.95	5.19
0.557	1.88	5.12
0.63	1.83	5.12
0.706	1.75	5.03
0.778	1.77	5.19
0.863	1.76	5.35
0.926	1.66	5.12

R_L (k Ω)	i_L (A)	V_o (V)
0.988	1.64	5.16
1.036	1.61	5.17

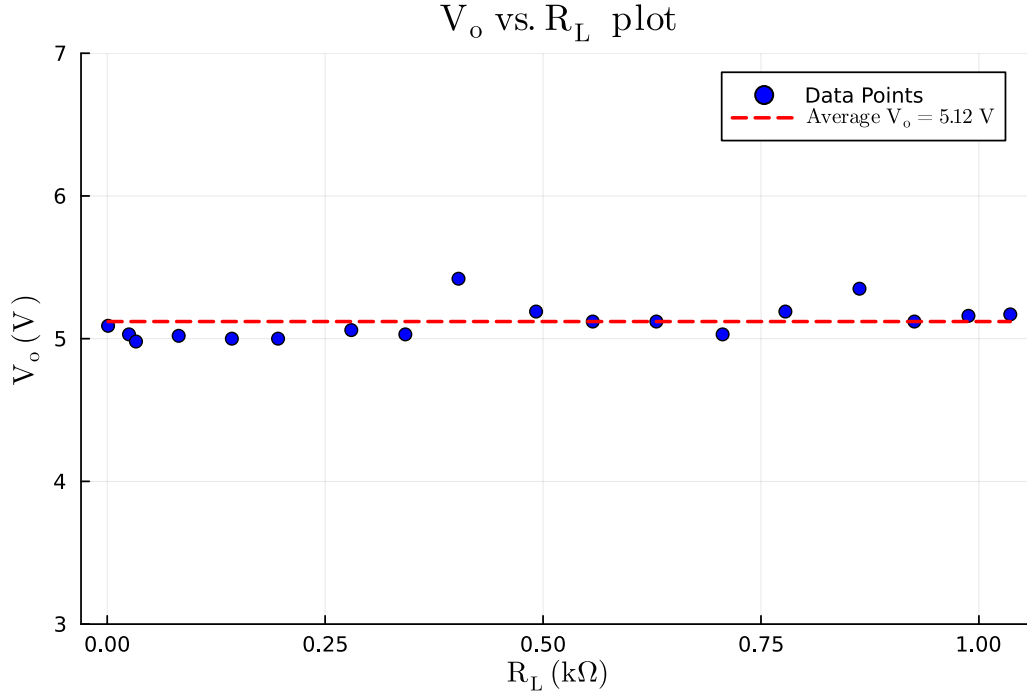In the following plot, we plotted input voltage with respect to output voltage.



From this graph we see that output voltage remains almost for different values of load resistance. Average value of the voltage is 5.12 V. The expected value is 5 V for IC7805.

4 Conclusion

In this experiment we studied different regulations for Zener diode. From line regulation, the breakdown voltage of the Zener diode was found be 6.55 V. In load regulation we got an understanding of what should be the load resistance for which the Zener diode reaches breakdown region.

In Zener diode the regulation is not perfect. We see that for IC7805, we get as stable output voltage 5 V for input voltage 6 V. While in Zener diode, with increasing current the voltage increases slightly. But in IC we found out that the voltage was really stable as expected.