

Experiment 05: Study of 555 Timer IC

Sagnik Seth - 22MS026
(Subgroup - A7)

1 Aim

To study the use of 555 Time IC as an astable multivibrator.

2 Theory

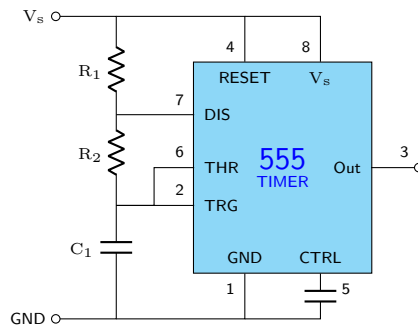


Figure 1: Circuit Diagram of 555 Timer IC

3 Data and Calculation

4 Sources of Error

5 Discussion and Conclusion