

Experiment 04: Study of Boolean Algebra

Sagnik Seth - 22MS026
(Subgroup - A7)

1 Aim

To study the basic laws of Boolean Algebra and verify them using implementation of logic gates using Integrated Circuits.

2 Theory

Boolean Algebra deals with logical operations of binary variables. A Boolean function f is generally defined as $f : \{0, 1\}^k \rightarrow \{0, 1\}$, that is, it takes input from k cartesian products of the set $\{0, 1\}$ and returns a single output which can be 0 or 1. The basic boolean functions are:

- NOT Gate

It is a unary operator which takes a single input and returns the negation of the input. It is represented by the symbol \bar{A} . If input is 1, it return 0 and if input is 0, it returns 1.

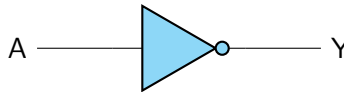


Figure 1: Representation of NOT Gate

- AND Gate

It is a binary operator which takes two inputs and returns the logical AND of the inputs. It is represented by the symbol $A \cdot B$. It returns 1 only if both inputs are 1, otherwise it returns 0.

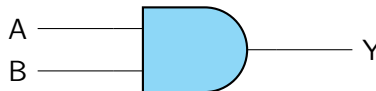


Figure 2: Representation of AND Gate

- OR Gate

It is a binary operator which takes two inputs and returns the logical OR of the inputs. It is represented by the symbol $A + B$. It returns 1 if any of the inputs is 1, otherwise it returns 0.

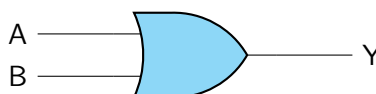


Figure 3: Representation of OR Gate

• XOR Gate

It is a binary operator which takes two inputs and returns the logical XOR of the inputs. It is represented by the symbol $A \oplus B$. It can be showed that the expression for XOR is equivalent to $\overline{A}B + A\overline{B}$. It returns 1 if the inputs are different, otherwise it returns 0.

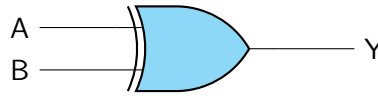


Figure 4: Representation of XOR Gate

• NAND Gate

It is a binary operator which takes two inputs and returns the logical NAND of the inputs. It is represented by the symbol \overline{AB} . Thus, it is a composition of AND and NOT operations. From de Morgan's law, it can be shown that NAND is equivalent to $\overline{A} + \overline{B}$.

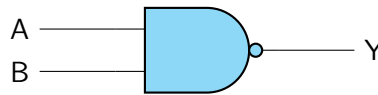


Figure 5: Representation of NAND Gate

- **NOR Gate** It is a binary operator which takes two inputs and returns the logical NOR of the inputs. It is represented by the symbol $\overline{A + B}$. Thus, it is a composition of OR and NOT operations. From de Morgan's law, it can be shown that NOR is equivalent to $\overline{A} \cdot \overline{B}$.

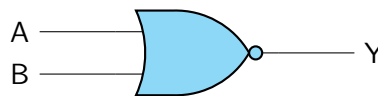


Figure 6: Representation of NOR Gate

A	B	AB	$A + B$	\overline{AB}	$\overline{A + B}$	$A \oplus B$
0	0	0	0	1	1	0
0	1	0	1	1	0	1
1	0	0	1	1	0	1
1	1	1	1	0	0	0

Table 1: Truth Table for the above logical operations

3 Verification of Truth Tables and Observations

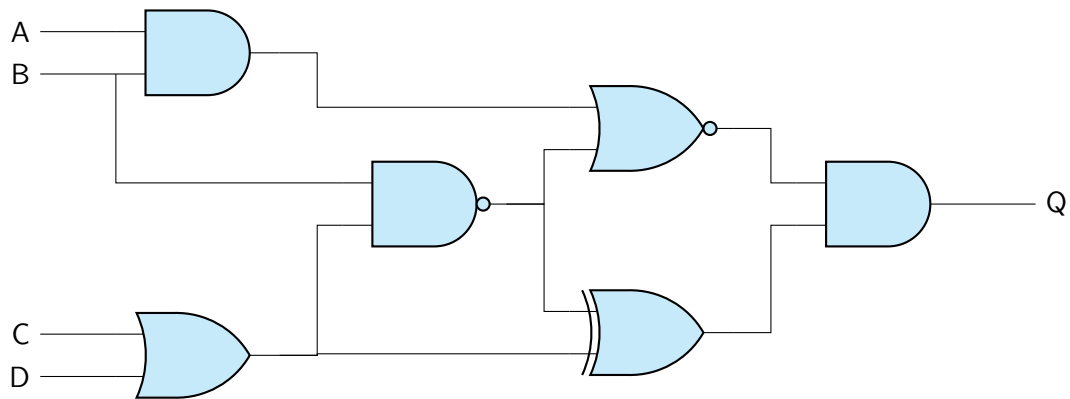


Figure 7: Logic Gate circuit diagram for for Example 1

Table 2: Truth Table for $Y = \overline{A}B(C + D)$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

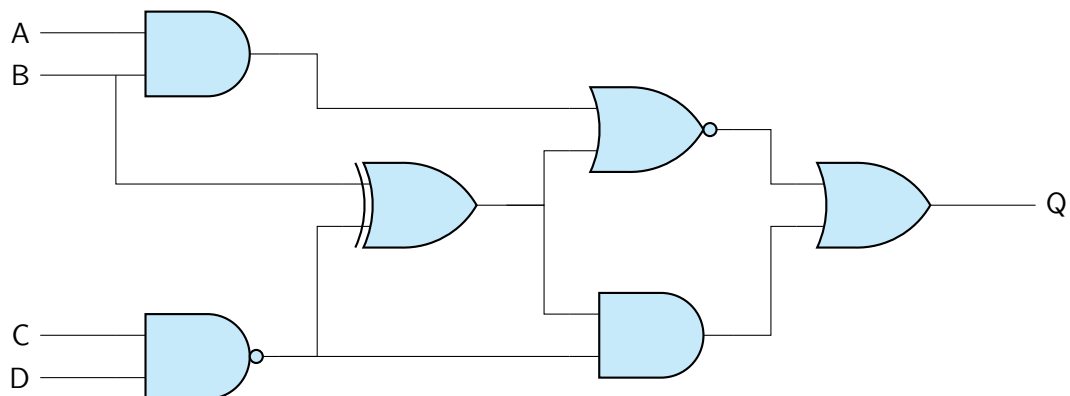


Figure 8: Logic Gate circuit diagram for for Example 2

Table 3: Truth Table for $Y = \overline{A}\overline{C} + \overline{A}\overline{D} + \overline{B}$

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

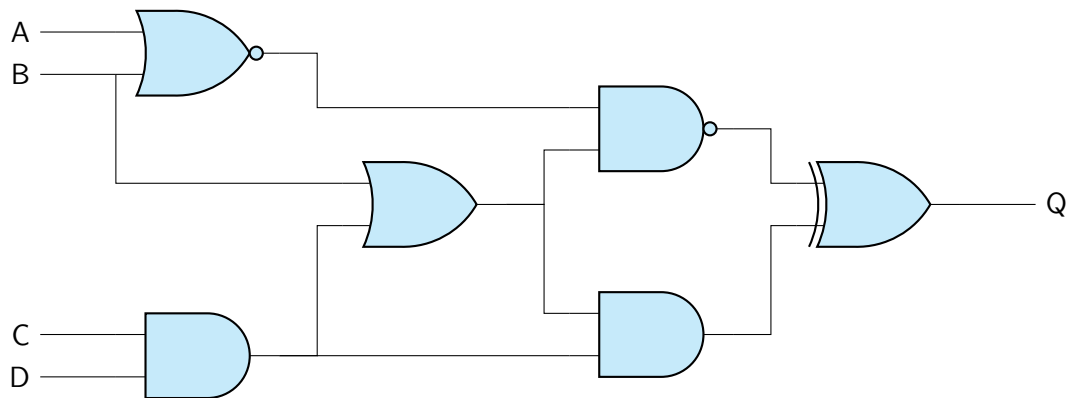
**Figure 9:** Logic Gate circuit diagram for for Example 3

Table 4: Truth Table for $Y = \overline{A}\overline{B} + \overline{D} + \overline{C}$

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

4 Sources of Error

5 Discussion and Conclusion